WORKSHEET I INTRODUCTION TO MICROCONTROLLER

ANSWER SCHEME

PART A: DIFFERENCE BETWEEN MICROCONTROLLER AND MICROPROCESSOR

1. State the difference between microcontroller and microprocessor

Microcontroller	Microprocessor
Can be treated as a small computer	1. It is the CPU in a computer
2. Contains CPU, RAM, ROM dan I/O devices in a single chip.	2. Contains only CPU in the chip.

- 2. Microcontroller system is like the human NERVOUS system.
- 3. Microcontroller receives **INPUT** and gives out OUTPUT.
- 4. Microcontroller processes information based on the **PROGRAMMING** in it.
- 5. Microcontroller keeps the programming in its system once uploaded. It only requires POWER for it to work.

WORKSHEET I INTRODUCTION TO MICROCONTROLLER

ANSWER SCHEME

PART B: PARTS IN A MICROCONTROLLER

1. Match the parts of a microcontroller and its function


CPU	\ /	Use to produce frequencies for
RAM & ROM		Provides power to the microcon-
Serial input/output	\	Receives information and pro- gram for it top process input and
Timing circuit		Allows the microcontroller to con- trol the system based on its in-
Timer / Crystal		Connects to input and output devices such as LED, motors and sensors
Devices		There are two types of signals-
Power supply	<u>/</u>	Memory spaces to store infor-

WORKSHEET I INTRODUCTION TO MICROCONTROLLER


ANSWER SCHEME

PART C: SCHEMATIC DIAGRAM

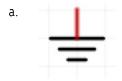- 1. Guides to drawing a good schematic diagram.
- a. Ensures that all lines drawn are STRAIGHT
- b. Ensures that all lines are not ARROW.
- c. Ensures that all lines drawn are HORIZONTALLY or VERTICALLY only.
- d. Minimize lines CROSSING each other to avoid confusion
- e. Use standardized SYMBOLS to represent each componnets.
- f. Ensures that all components in the diagram are LABELLED
- 2. What does each of the following symbol means?:



NEGATIVE TERMINAL / GROUND IN A CIRCUIT

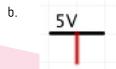

POWER SUPPLY

ANSWER SCHEME

PART A: OUTPUT CIRCUIT PROGRAMMING

A) Answer the following question:

- 1. Arduino runs two programs-which are SETUP and LOOP
- 2. There are two types of signals that can be sent and received by Arduino, which are DIGITAL signals and ANALOG signals.
- 3. To use pin 8 to turn on the LED, pin 8 needs to be set as **OUTPUT** with the program command **pinMode(8,OUTPUT)**
- 4. pinMode(5, OUTPUT) sets pin 5 to become OUTPUT
- 5. digitalWrite(13, HIGH) will send digital signal HIGH to pin 13
- 6. analogWrite(7, 120) will send analog signal 120 to pin 7
- 7. The number 1000 in delay(1000) means 1000 MILLISECONDS
- 8. Each program line must end with the symbol: ;

OUTPUT

ANSWER SCHEME

B) State the function of the code, or the code for the function:

1. pinMode(5, INPUT) : SET PIN 5 AS INPUT

2. pinMode(8, OUTPUT) : Tetapkan pin 8 sebagai output

3. delay(1000) :WAIT 1000 MILLISECONDS / 1

SECONDS

4. **delay(100)** : Wait 0.1 second

5. digitalWrite(5, HIGH) : SEND DIGITAL SIGNAL HIGH TO

PIN 5

6. digitalWrite(8, LOW) : Send digital signal LOW to pin 8

7. analogWrite(3, 255) : SEND ANALOG SIGNAL 255 TO

PIN 3

8. analogWrite(4,100) : Send analog signal 100 to pin 4

B) Write the program for the following action:

1. Turn on LED connected to pin 5

```
1 void setup() {
2  pinMode(5, OUTPUT);
3  }
4
5 void loop() {
6  digitalWrite(5, HIGH);
7  }
```

ANSWER SCHEME

2. The LED connected to pin 6 will turn on for 3 seconds and turn off for 1 second.

```
10 void setup() {
2    pinMode(6, OUTPUT);
3  }
4
50 void loop() {
6    digitalWrite(6, HIGH);
7    delay(3000);
8    digitalWrite(6, LOW);
9    delay(1000);
10 }
```

OUTPUT

3. By using the red LED (pin 5), green LED (pin 6) and yellow LED (pin 7), create a traffic light program

```
1□ void setup() {
     pinMode (5, OUTPUT);
 3
   pinMode(6, OUTPUT);
    pinMode (7, OUTPUT);
 4
 5
   }
 6
 7□ void loop() {
 8
     digitalWrite(7, LOW);
 9
     digitalWrite(5, HIGH);
10
     delay(5000);
11
    digitalWrite(5, LOW);
12
   digitalWrite(6, HIGH);
   delay(5000);
13
14
    digitalWrite(6, LOW);
15
     digitalWrite(7, HIGH);
16
     delay(1000);
17
   }
```

ANSWER SCHEME

4. The LED connected to pin 9 will turn on with 50% brightness

```
1 void setup() {
2   pinMode(9, OUTPUT);
3  }
4
5 void loop() {
6   analogWrite(9, 123);
7  }
8
```

ANSWER SCHEME


5. Buzzer to play two different sounds

```
1 void setup() {
2   pinMode(8, OUTPUT);
3  }
4
5 void loop() {
6   tone(8, 250, 250);
7   delay(1000);
8   tone(8, 500, 250);
9   delay(1000);
10  }
```

ANSWER SCHEME


PART B: INTRODUCTION TO OUTPUT CIRCUIT CONNECTION AND SIMULATION

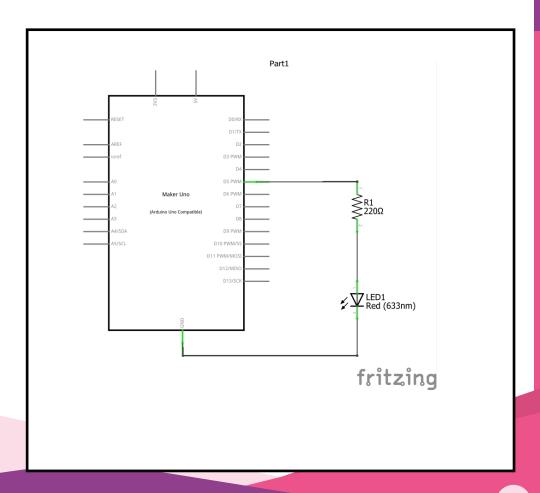- A) Draw the following schematic:
- 1. 1 LED connected to pin 5




ANSWER SCHEME

2. Buzzer connected to pin 8

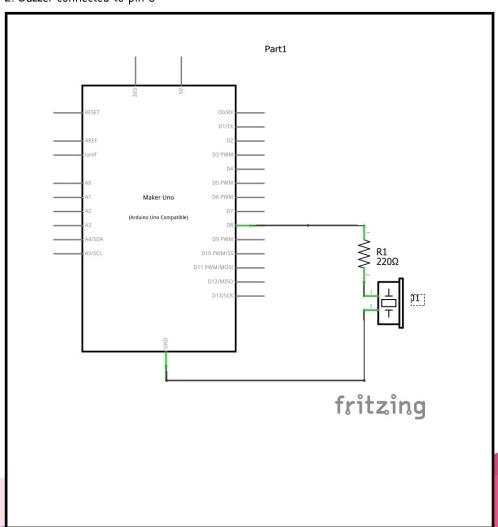

ANSWER SCHEME

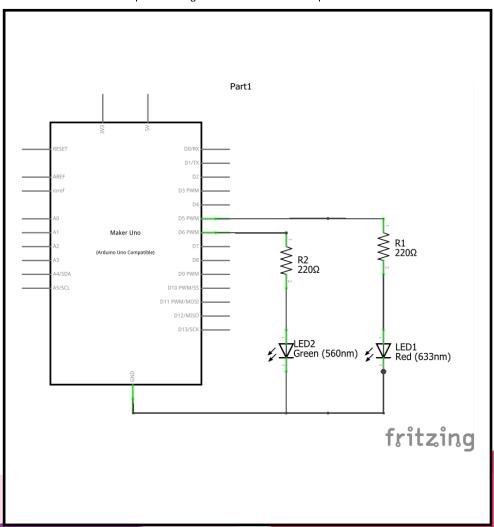3. Red LED connected to pin 5 and green LED connected to pin 6



ANSWER SCHEME

B) Simulate the circuit in Part A and produce the program that will perform the following action.

Write the project UR	RL for checking	
1) Circuit A1 -	Blinking LED	entis
2) Circuit A1	LED by and an with E00	reme
2) Circuit A1 -	LED turned on with 50	eduli
3) Circuit A2 -	Buzzer to r liftle the	gedlirement is
4) Circuit A3 -	that the accept	turn to turn on
5) Circ ans	affic light	
PUN		

WORKSHEET 3 INPUT

ANSWER SCHEME

PART A: INPUT CIRCUIT PROGRAMMING

- A) Answer the following question
- 1. To use pin 8 as input pin, the pin needs ot be set as INPUT with the programming command pinMode(8,INPUT)
- 2. analogRead can be used at pin A0-A5 only.
- 3. To open a communication channel between the computer and Arduino, we need to write Serial.begin(9600) at setup and Serial.println() in loop
- B) State the function of the code, or the code for the function
- 1. analogRead(A0)

A0

- 2. digitalRead(8)
- 3. x = analogRead(A0)pin A0 to the variable x
- z = digitalRead(5)

variable z

:Reads analog signals from pin

: Reads digital signals from pin 8

: Set the analog value read from

: Set the digital value read from pin 5 to the

INPUT

ANSWER SCHEME

- C) Write the program for the following function
- 1. Read the value received in analog pin A2 and display it through Serial communication

```
10 void setup() {
2    pinMode(A2, INPUT);
3    Serial.begin(9600);
4  }
5
60 void loop() {
7    int x = analogRead(A2);
8    Serial.println(x);
9    delay(200);
10 }
```

INPUT

ANSWER SCHEME


2. Read the value received in digital pin 5 and display it through Serial communication

WORKSHEET 3 INPUT

ANSWER SCHEME

PART B: INTRODUCTION TO INPUT CIRCUIT CONNECTION AND SIMULATION

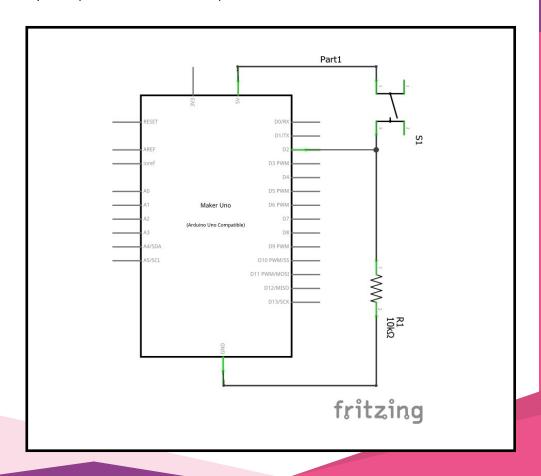
- A) Draw the schematic for the following circuit
- 1) 1 push button connected to pin 2



INPUT

ANSWER SCHEME


2) 1 potentiometer connected to pin A2

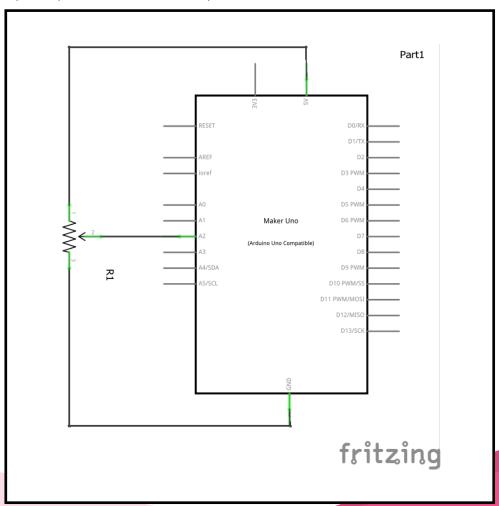

INPUT

ANSWER SCHEME

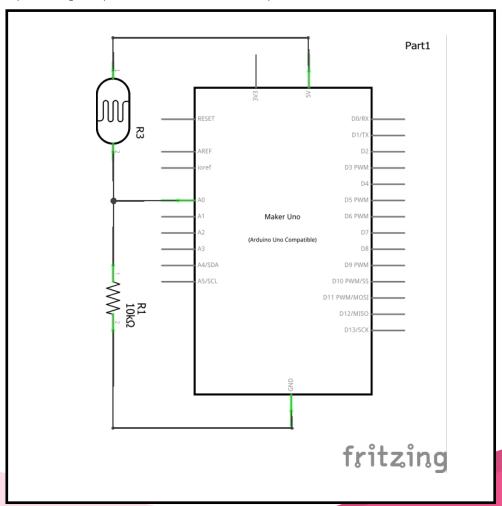3) 1 Light Dependent Resistor connected to pin A0



WORKSHEET 3 INPUT

ANSWER SCHEME

B) Simulate the circuit in A and produce the program that will perform action.

action.		.6
Write the project U	IRL for checking	o.nt.
1) Circuit A1 –	Read the pushbutton valueand dis	reduirement is with Serial
2) Circuit A2 – Communication		
3) Circuit A3 -	Read the Read that fulfils the accept	Serial Communication

136

ANSWER SCHEME

WORKSHEET 4 INPUT AND OUTPUT

PART A: INPUT AND OUTPUT PROGRAMMING

A) State the meaning of the following symbol:

1. > Bigger than

2. < : Smaller than

3. <= : Smaller than or equals to

4. >= : Bigger than or equals to

5. != : Not equals to

6. == : **Equals to**

- B) Write the program that performs the following function:
- 1) Read the pushbutton at pin 2. If it is pressed, turn on the LED at pin 5

```
10 void setup() {
2    pinMode(2, INPUT);
3    pinMode(5, OUTPUT);
4    Serial.begin(9600);
5  }
6  
70 void loop() {
8    int x = digitalRead(5);
9    Serial.println(x);
100 if(x == 1) {
11    digitalWrite(5, HIGH);
120 } else {
13    digitalWrite(5, LOW);
14 }
15 }
```

WORKSHEET 4 INPUT AND OUTPUT ANSWER SCHEME


2) Read the light dependent resistor connected to pin AO. If the value read is more than or equals to 500, turn off the LED at pin 5 and 6.

```
1 void setup() {
     pinMode (A0, INPUT);
     pinMode (5, OUTPUT);
     pinMode (6, OUTPUT);
     Serial.begin (9600);
 5
 6
   }
 7
 8 void loop() {
      int x = analogRead(A0);
 9
     Serial.println(x);
10
    if(x >= 500) {
11⊟
12
       digitalWrite(5, LOW);
      digitalWrite(6, LOW);
13
     } else {
14⊟
      digitalWrite(5, HIGH);
15
      digitalWrite(6, HIGH);
16
17
     }
18
    }
19
```

ANSWER SCHEME


PART B: INTRODUCTION TO INPUT AND OUTPUT CIRCUIT CONNECTION AND SIMULATION

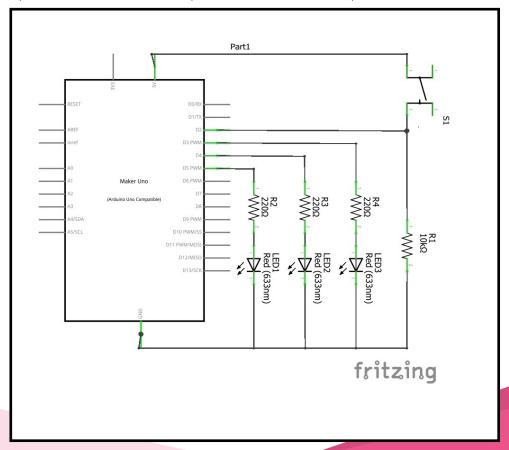- A) Draw the following schematic:
- 1) Push button connected to pin 2 and 3 LED connected to pin 3,4 and 5



ANSWER SCHEME

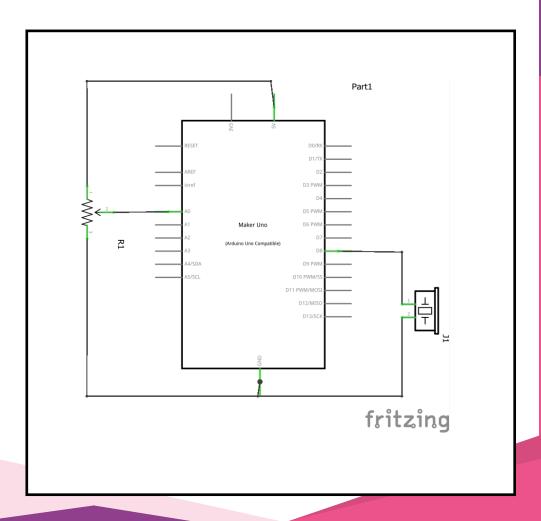2) Potentiometer connected to pin AO and buzzer connected to pin 8



ANSWER SCHEME

B) Simulate the circuit in A and produce the program that will perfectly action.
Write the project URL for checking
1) Circuit A1 - Read the pushbutton. If the pushbase at pin 3 and 4. Or else, turn on the LED at pin 5.
Le real
B) Simulate the circuit in A and produce the program that will perfect the following action. Write the project URL for checking 1) Circuit A1 - Read the pushbutton. If the pushbut at pin 3 and 4. Or else, turn on the LED at pin 5. 2) Circuit A2 - Read the pushbutton. If the pushbut the LEDs. Or else, turn off all the LEDs. 3) Circuit A3 - Read the pushbutton at the LEDs. 2) Circuit A3 - Read the pushbutton at the LEDs. 4. Provide the project URL for checking the pushbutton at pin 5. 2) Circuit A2 - Read the pushbutton at pin 5. 2) Circuit A3 - Read the pushbutton at pin 5. 3) Circuit A3 - Read the pushbutton at pin 5. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the pushbutton at pin 6. 4. Provide the pushbutton at pin 6. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the project URL for checking the pushbutton at pin 6. 4. Provide the pushbutton at pin 6. 4. Pr
wat to accel
3) Circuit A3 - Response potentiometer value is more than 250, play sound on the
IN ans

ANSWER SCHEME

By using the components provided, choose and make one:

- Alarm that will be activated when the door is opened 1)
- 2) Music box
- 3) LEDs that will be turned on when it is night time

For each project, you need to produce the following docu

- 1. Block diagram for project design
- 2. Schematic diagram for the circuit
- Any answer that fulfils the requirement is 3. Program for the circuit and ose the program strucutre
- Simulation on tinkerlab 4.
- 5. Actual functioning
- Recommendation 6.

Collect all the evidences